




# ***DSL*Lab. 08    Combinational Logic**

# Lab. 08 Combinational Logic

- Design and verify the following circuits using Verilog HDL and Schematic
- Verilog
  - ◆ Behavioral level modeling
  - ◆ Dataflow modeling
  - ◆ Structural level modeling
- Schematic
- Please write and upload the lab report (Lab08) -- Due on 2022/10/28 23:59


# 4-bit Ripple-Carry Adder

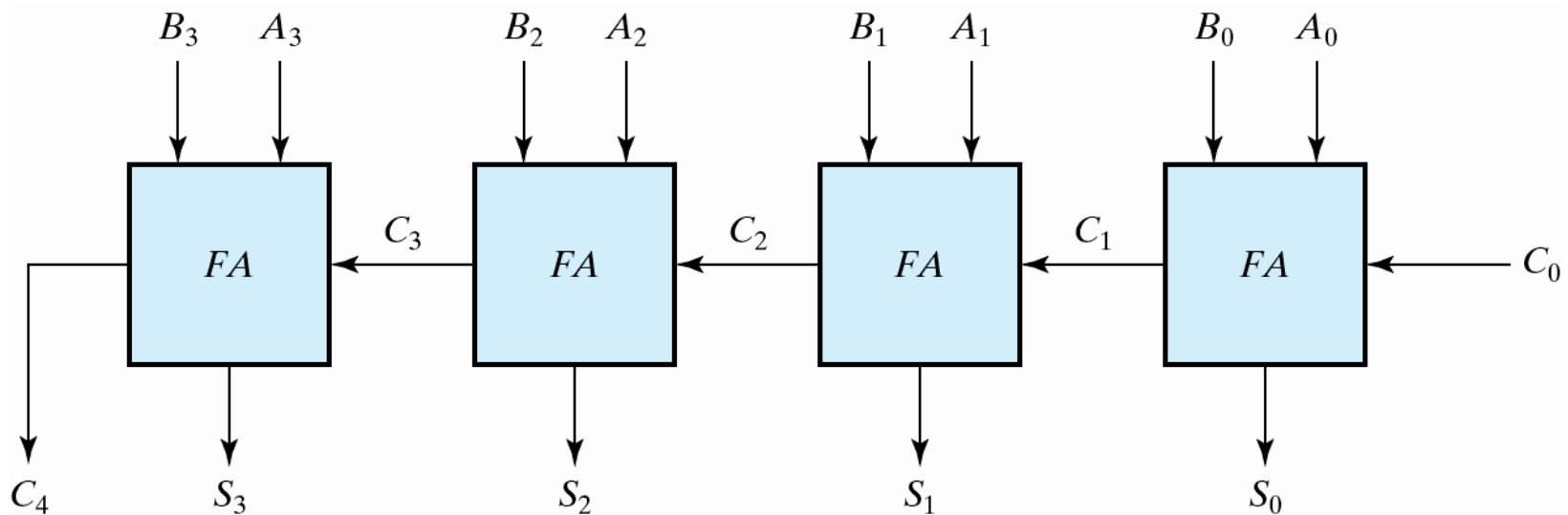
 
# Gate-level Description of 4-bit Ripple-Carry Adder

```
module half_adder (output S, C, input x, y);
    xor (S, x, y);
    and (C, x, y);
endmodule
```


```
module full_adder (output S, C, input x, y, z);
    wire S1, C1, C2;
    half_adder HA1 (S1, C1, x, y);
    half_adder HA2 (S, C2, S1, z);
    or G1 (C, C2, C1);
endmodule
```



```
module ripple_carry_4_bit_adder ( output [3:0] Sum, output C4, input [3:0] A, B, input C0);
    wire C1, C2, C3; // Intermediate carries
```

```
    full_adder FA0 (Sum[0], C1, A[0], B[0], C0),
    full_adder FA1 (Sum[1], C2, A[1], B[1], C1),
    full_adder FA2 (Sum[2], C3, A[2], B[2], C2),
    full_adder FA3 (Sum[3], C4, A[3], B[3], C3);
```

```
endmodule
```

 

# Exercise 1: BCD to Excess-3 Code Converter (1/3)

## BCD to Excess-3 Code Converter

**Table 4.2**

*Truth Table for Code-Conversion Example*

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

# Exercise 1: BCD to Excess-3 Code Converter (2/3)

## ■ The simplified functions (Circuit 1)


- ◆  $z = D'$
- ◆  $y = CD + C'D'$
- ◆  $x = B'C + B'D + BC'D'$
- ◆  $w = A + BC + BD$

## ■ Another implementation (Circuit 2)

- ◆  $z = D'$
- ◆  $y = CD + C'D' = CD + (C + D)'$
- ◆  $x = B'C + B'D + BC'D' = B'(C + D) + B(C + D)'$
- ◆  $w = A + BC + BD = A + B(C + D)$

## ■ Draw the logic diagrams of Circuit 1 and Circuit 2, and then verify Circuit 1 = Circuit 2 (using Verilog Dataflow modeling)
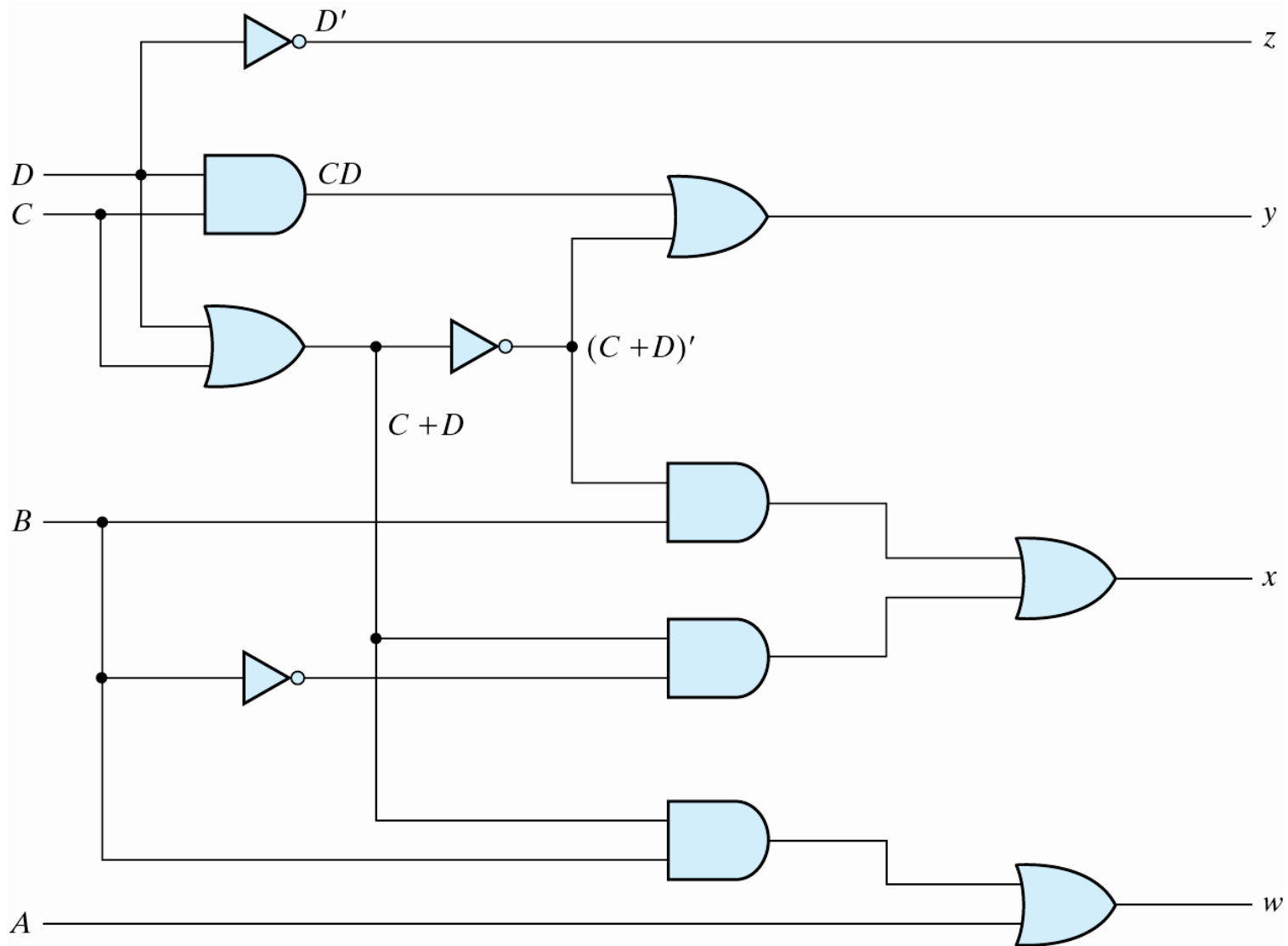
# Exercise 1: BCD to Excess-3 Code Converter (3/3)




## Exercise 2: Full-Adder (1/2)

- Derive the following Boolean functions using Karnaugh maps
- $S = z \oplus (x \oplus y)$ ,  $C = xy + xz + yz$  (Circuit 1)
- Draw the logic diagram of Circuit 1

**Table 4.4**  
*Full Adder*



<i>x</i>	<i>y</i>	<i>z</i>	<b>C</b>	<b>S</b>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


  
## Exercise 2: Full-Adder (2/2)

- Derive the following Boolean functions using Karnaugh maps
- $S = z \oplus (x \oplus y)$ ,  $C = z(x \oplus y) + xy$  (Circuit 2)
- Draw the logic diagram of Circuit 2
- Verify Circuit 1 = Circuit 2  
(using Verilog Structural level modeling)



## Exercise 3: 8-bit Ripple-carry Adder

- Design and verify the 8-bit ripple-carry adder composed of eight full-adders (using Verilog **Structural level modeling**)

