



DSLab. 15 Memory

Lab. 15 Memory

- Design and Verify the following circuits using Verilog HDL
 - ◆ 4 x 4 RAM (Structural modeling)
 - ◆ 8 x 8 Register File (Behavioral modeling)


- Please write and upload the lab report (Lab15) -- Due on 2022/12/16 23:59

Example 1: 4-bit ripple counter (1/2)


Table 6.4
Binary Count Sequence

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

Fig. 6.8
Four-bit binary ripple counter

 

(a) With T flip-flops

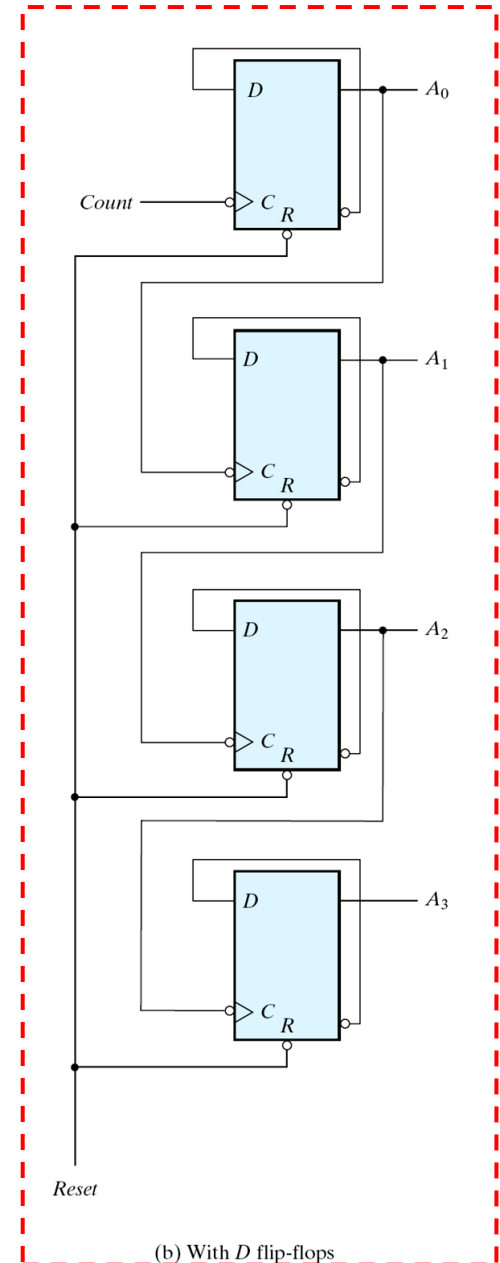

(b) With D flip-flops

Example 1: 4-bit ripple counter (2/2)

Structural model

```
`timescale 1ns / 100 ps
```

```
module Ripple_Counter_4bit (A3,A2,A1,A0, Count, Reset);
```

```
    output A3,A2,A1,A0;
```

```
    input Count,Reset;
```

```
//Instantiate complementing flip-flop
```

```
    Comp_D_flip_flop F0 (A0, Count, Reset);
```

```
    Comp_D_flip_flop F1 (A1, A0, Reset);
```

```
    Comp_D_flip_flop F2 (A2, A1, Reset);
```

```
    Comp_D_flip_flop F3 (A3, A2, Reset);
```

```
endmodule
```

```
//Complementing flip-flop with delay
```

```
//Input to D flip-flop = Q'
```

```
module Comp_D_flip_flop (Q, CLK, Reset);
```

```
    output Q;
```

```
    input CLK, Reset;
```

```
    reg Q;
```

```
    always @ (negedge CLK, posedge Reset)
```

```
        if (Reset) Q <= 1'b0; else Q <= #2 ~Q;
```

```
endmodule
```

```
//Stimulus for testing ripple counter
```

```
module testcounter;
```

```
    reg Count;
```

```
    reg Reset;
```

```
    wire A0,A1,A2,A3;
```

```
//Instantiate ripple counter
```

```
    Ripple_Counter_4bit M0 (A3, A2, A1, A0, Count, Reset);
```

```
    always
```

```
        #5 Count = ~Count;
```

```
    initial
```

```
        begin
```

```
            Count = 1'b0;
```

```
            Reset = 1'b1;
```

```
            #4 Reset = 1'b0;
```

```
        end
```

```
    initial #170 $finish;
```

```
endmodule
```

Example 2: 64 x 4 memory (1/3)

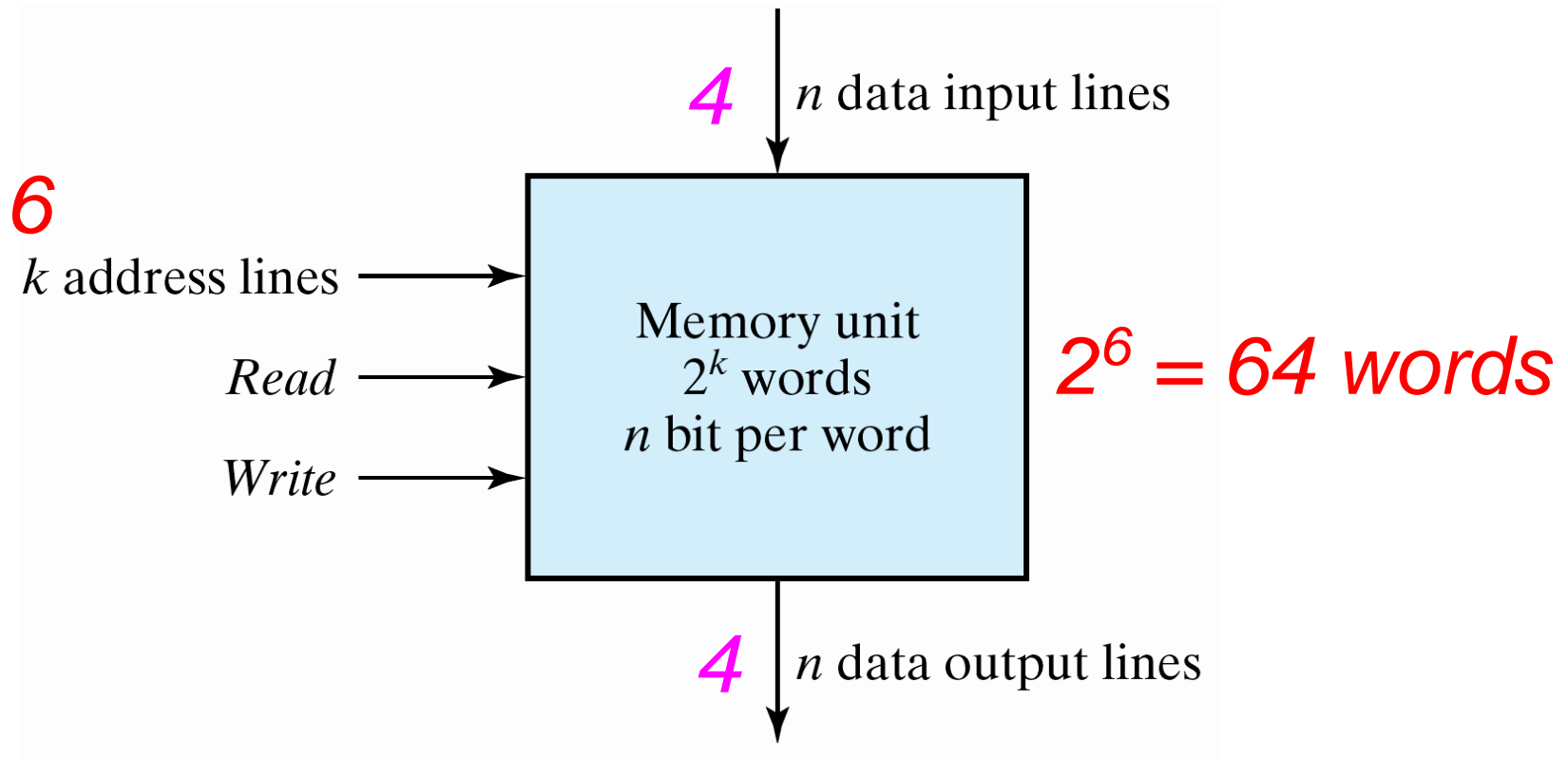


Fig. 7.2 Block diagrams of a memory unit

Example 2: 64 x 4 memory (2/3)

Behavioral model

```
module memory (Enable, ReadWrite, Address, DataIn, DataOut);  
    input          Enable, ReadWrite;  
    input  [3: 0]   DataIn;  
    input  [5: 0]   Address;  
    output [3:0]    DataOut;  
    reg     [3: 0]   DataOut;  
    reg     [3: 0]   Mem [0: 63];           //64 x 4 memory  
  
    always @ (Enable or ReadWrite or Address)  
    if (Enable)  
        if (ReadWrite) DataOut = Mem[Address]; //Read  
        else Mem[Address] = DataIn;           //Write  
        else DataOut = 4'bz;                   //High impedance state  
endmodule
```

Example 2: 64 x 4 memory (3/3)

```
module t_memoryt;
    reg    t_Enable, t_ReadWrite;
    reg    [3: 0] t_DataIn;
    reg    [5: 0] t_Address;
    wire   [3:0] t_DataOut;

    memory M0 (t_Enable, t_ReadWrite, t_Address, t_DataIn, t_DataOut);
    initial #150 $finish;

    initial begin
        t_Enable = 1;
        t_ReadWrite = 0;
        t_Address = 0;
        t_DataIn = 0;

        #10 t_ReadWrite=1'b0;    //Write
        #10 t_Address =5'b00001; t_DataIn =4'b0001;
        #10 t_Address =5'b00010; t_DataIn =4'b0010;
        #10 t_Address =5'b00011; t_DataIn =4'b0011;
        #10 t_Address =5'b00100; t_DataIn =4'b0100;
        #10 t_Address =5'b00101; t_DataIn =4'b0101;
        #10 t_Address =5'bxxxxx; t_DataIn =4'bxxxx;
        #10 t_ReadWrite=1'b1;    //Read
        #10 t_Address =5'b00001;
        #10 t_Address =5'b00010;
        #10 t_Address =5'b00011;
        #10 t_Address =5'b00100;
        #10 t_Address =5'b00101;
    end
endmodule
```

Example 3: 8 x 8 Register file with 2 read and 1 write ports

```
module regfile(WA, WE, RAA, REA, RAB, REB, DATA_W, DATA_A, DATA_B, clk, rst);
```

```
input [2:0] WA, RAA, RAB;
```

```
input WE, REA, REB, clk, rst;
```

```
input [7:0] DATA_W;
```

```
output [7:0] DATA_A, DATA_B;
```

```
reg [7:0] DATA_A, DATA_B;
```

```
reg [7:0] registers[7:0];
```

```
assign DATA_A = registers[RAA];
```

```
assign DATA_B = registers[RAB];
```

```
always @ (posedge clk or negedge rst)
begin
```

```
    if (~rst)
```

```
        registers[0] = 0;
```

```
    else
```

```
        begin
```


```
            if (WE) registers[WA] <= DATA_W;
```

```
        end
```

```
    end
```

```
endmodule
```

Behavioral model

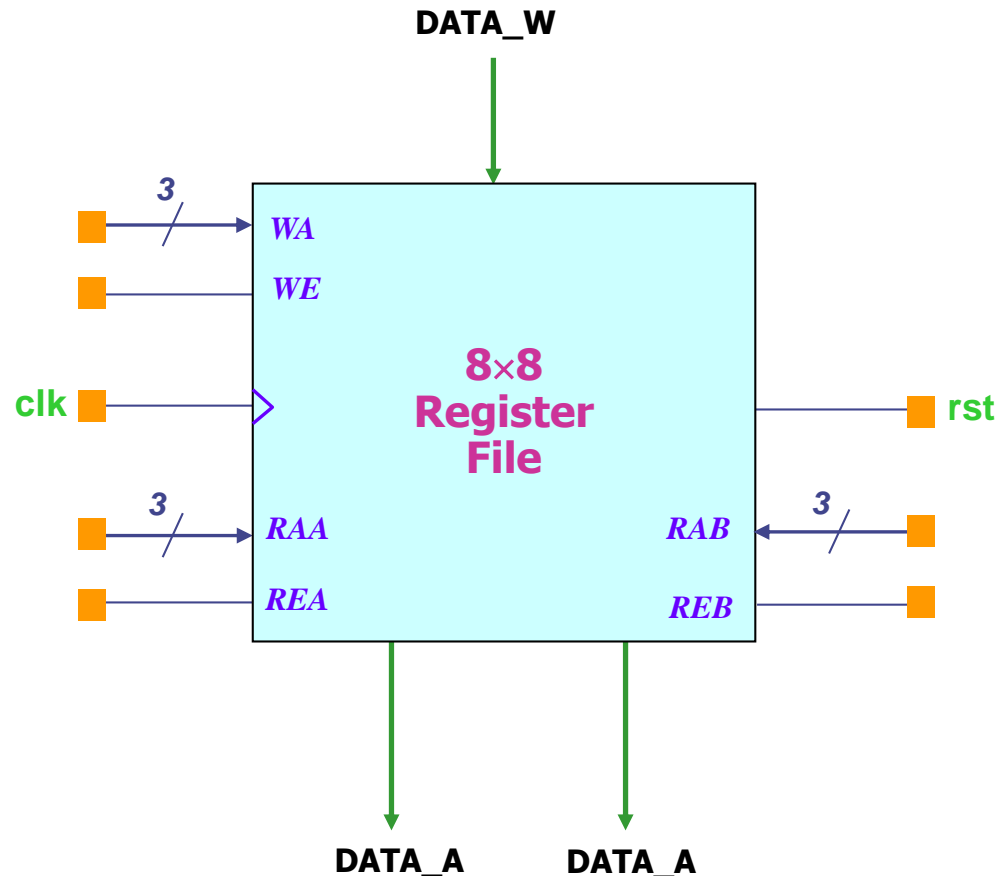

Example 4: 4 x 16 decoder

```
module decoder_case (binary_in, decoder_out , enable);  
    input [3:0] binary_in ;           // 4 bit binary input  
    input  enable ;                   // Enable for the decoder  
    output [15:0] decoder_out ;       // 16-bit out
```

```
    reg [15:0] decoder_out ;
```

```
    always @ (enable or binary_in)  
    begin
```

```
        decoder_out = 0;
```

```
        if (enable) begin
```

```
            case (binary_in)
```

```
                4'h0 : decoder_out = 16'h0001;
```

```
                4'h1 : decoder_out = 16'h0002;
```

```
                4'h2 : decoder_out = 16'h0004;
```

```
                4'h3 : decoder_out = 16'h0008;
```

```
                4'h4 : decoder_out = 16'h0010;
```

```
                4'h5 : decoder_out = 16'h0020;
```

```
                4'h6 : decoder_out = 16'h0040;
```

```
                4'h7 : decoder_out = 16'h0080;
```

```
                4'h8 : decoder_out = 16'h0100;
```

```
                4'h9 : decoder_out = 16'h0200;
```

```
                4'hA : decoder_out = 16'h0400;
```

```
                4'hB : decoder_out = 16'h0800;
```

```
                4'hC : decoder_out = 16'h1000;
```

```
                4'hD : decoder_out = 16'h2000;
```

```
                4'hE : decoder_out = 16'h4000;
```

```
                4'hF : decoder_out = 16'h8000;
```

```
            endcase
```

```
        end
```

```
    end
```

```
endmodule
```

Behavioral model

```
module decoder_assign (binary_in, decoder_out , enable);  
    input [3:0] binary_in ;           // 4 bit binary input  
    input  enable ;                   // Enable for the decoder  
    output [15:0] decoder_out ;       // 16-bit out
```

```
    wire [15:0] decoder_out ;
```

```
    assign decoder_out = (enable) ? (1 << binary_in) : 16'b0 ;
```

```
endmodule
```

Exercise 1: 4 x 4 RAM (1/2)

■ Design and verify the 4 x 4 RAM using Verilog HDL

◆ Structural modeling

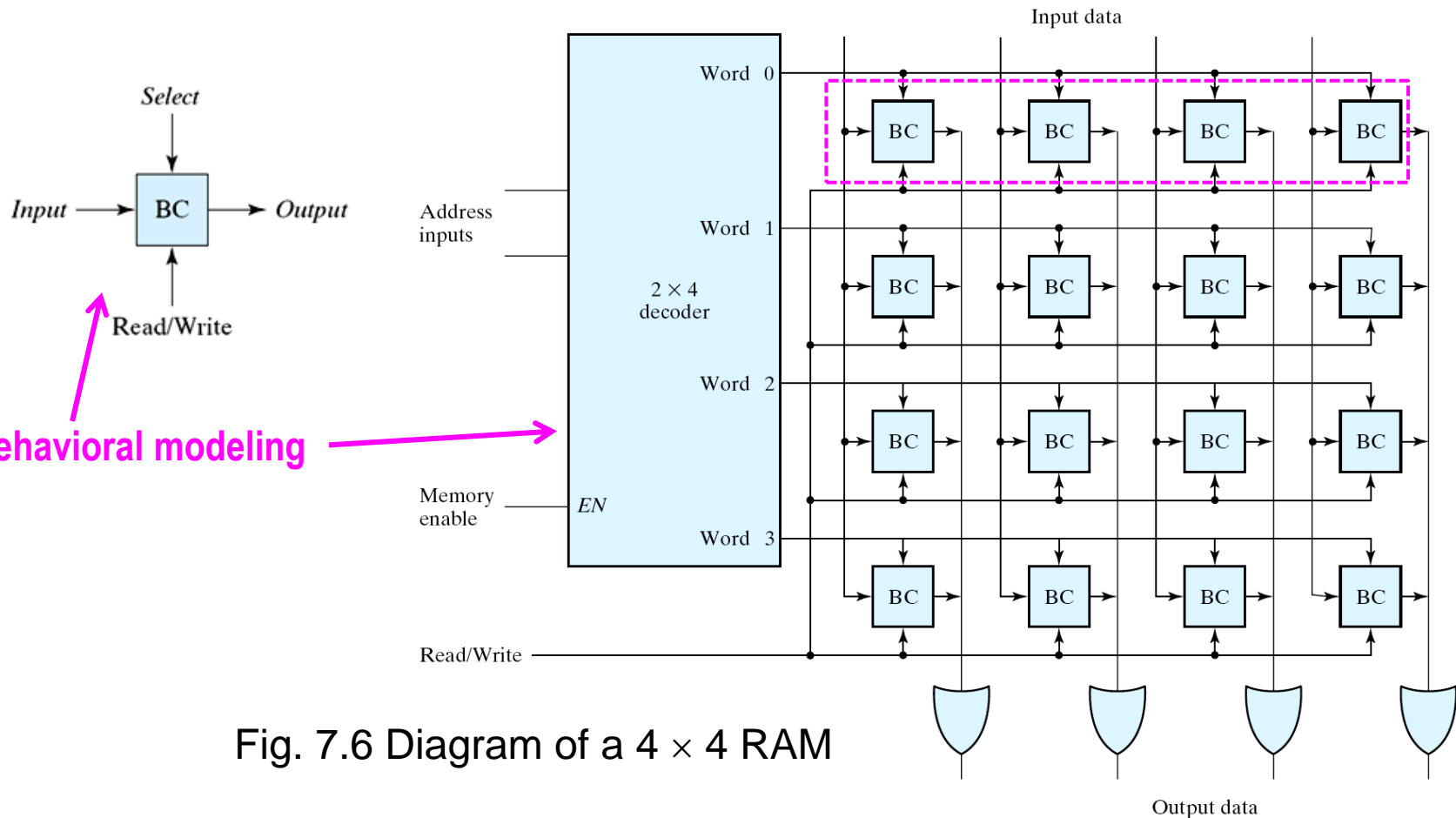


Fig. 7.6 Diagram of a 4 x 4 RAM

Exercise 1: 4 x 4 RAM (2/2)

- The memory unit BC can be described using **behavioral modeling**

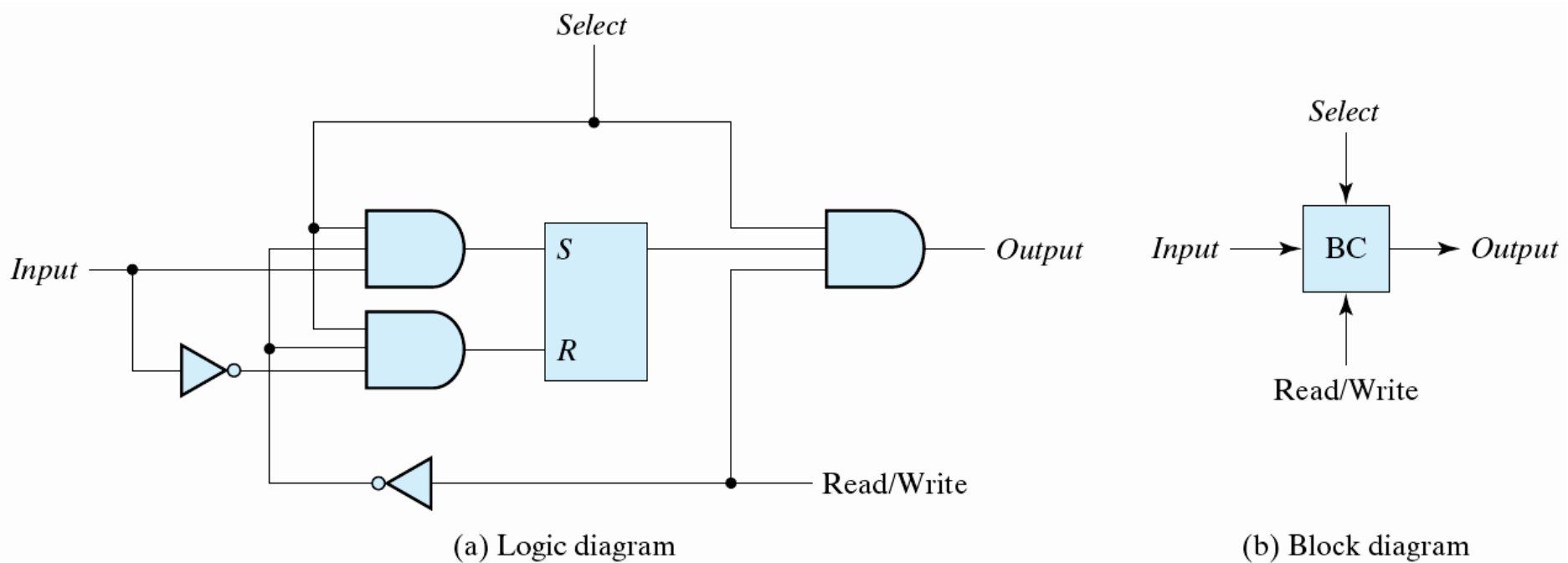


Fig. 7.5 Memory cell

Exercise 2: 8 x 8 Register File (1/2)

- Register file is used as fast temporary storage
- Design and verify the 8 x 8 register file with 2 read ports and 1 write port using Verilog HDL
 - ◆ Behavioral modeling

Exercise 2: 8 x 8 Register File (2/2)

