



# ***DSLAb. 11 D Latch and D Flip-Flops***

# Lab. 11 D Latch and D Flip-Flops

- Design and Verify the following circuits using Verilog HDL
  - ◆ D Latch
  - ◆ D Flip-Flops
- Verilog
  - ◆ Behavioral level modeling
  - ◆ Dataflow modeling
  - ◆ Structural level (Gate-level) modeling
- Please write and upload the lab report (Lab11) -- Due on 2022/11/18 23:59

# Behavioral Description of D Latch

```
module D_latch (Q, D, En);  
    output Q;  
    input D, En;  
    reg Q;
```

```
    always @ (En, D)  
        if (En) Q <= D;      // Alternative: if (En == 1) Q <= D;  
endmodule
```

 


Fig. 5.6 D latch

(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table

# Behavioral Description of D Flip-Flop

```
module D_flip_flop (Q, D, Clk);  
    output    Q;  
    input     D, Clk;  
    reg       Q;  
  
    always @ (negedge Clk)  
        Q <= D;  
endmodule
```


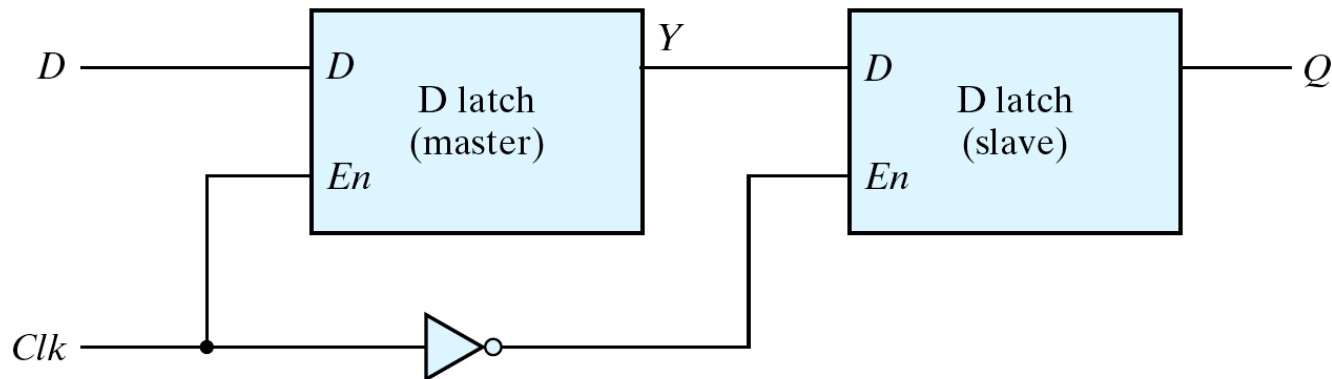


Fig. 5.9 Master-slave *D* flip-flop

# D Flip-Flop with asynchronous reset (1/2)
 
## Behavioral Description of D Flip-Flop with asynchronous reset

```
module D_flip_flop_AR_b (Q, Q_b, D, Clk, rst);  
    output Q, Q_b;  
    input  D, Clk, rst;  
    reg    Q;  
  
    assign Q_b = ~Q;  
    always @ (posedge Clk, negedge rst)  
        if (rst == 0) Q <= 1'b0;  
        else Q <= D;  
endmodule
```



(b) Graphic symbol

<i>R</i>	<i>Clk</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(b) Function table

## D Flip-Flop with asynchronous reset (2/2)

```
module t_D_flip_flops;
    wire Q, Q_b;
    reg D, Clk, rst;

    D_flip_flop_AR_b M0 (Q, Q_b, D, Clk, rst);

    initial #100 $finish;
    initial begin Clk = 0; forever #5 Clk = ~Clk; end
    initial fork
        D = 1;
        rst = 1;
        #20 D = 0;
        #40 D = 1;
        #50 D = 0;
        #60 D = 1;
        #70 D = 0;
        #90 D = 1;
        #42 rst = 0;
        #72 rst = 1;
    join
endmodule
```

# Exercise 1: D Latch

■ Design and verify the D latch using Verilog HDL

◆ Structural level (Gate-level) modeling

 


Fig. 5.6 D latch


(a) Logic diagram

$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table
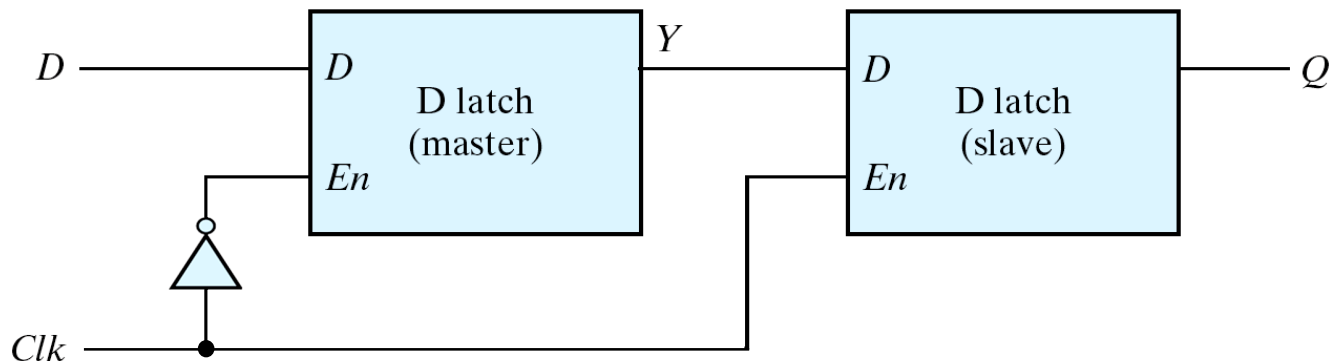
## Exercise 2: Master-slave D Flip-Flop

- Design and verify the positive-edge-triggered master-slave D flip-flop using Verilog HDL
  - ◆ Structural level (Gate-level) modeling



$Clk$	$D$	$Q$	$Q'$
$\uparrow$	0	0	1
$\uparrow$	1	1	0



(b) Function table

Fig. Positive-edge-triggered master-slave D flip-flop


 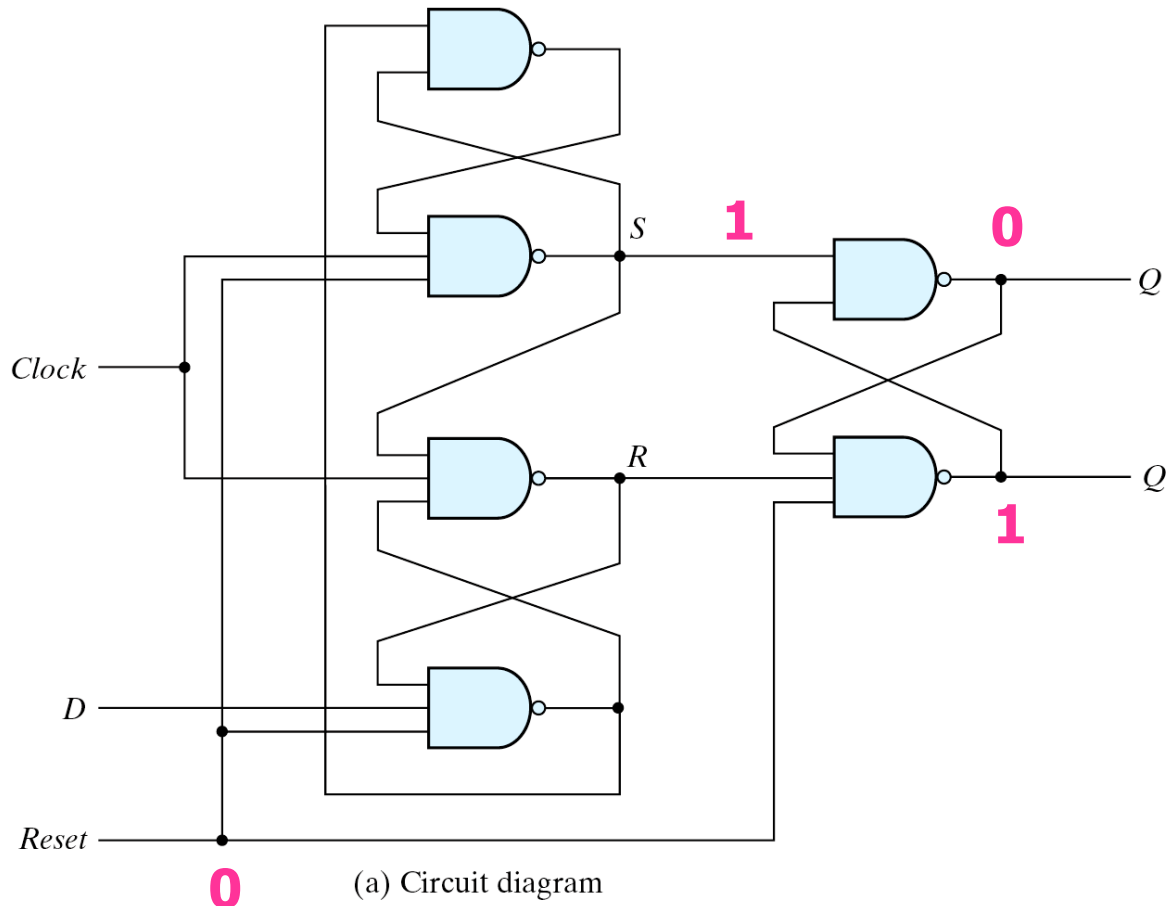
## Exercise 3: D flip-flop with asynchronous reset

- Design and verify the *D* flip-flop with asynchronous reset shown in Fig. 5.14 using Verilog HDL (Gate-level modeling)



<i>R</i>	<i>Clk</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(b) Function table

Fig. 5.14 *D* flip-flop with asynchronous reset