





DSLAb. 05 Digital Logic Gates & Karnaugh Map

Lab. 5 Digital Logic Gates & Karnaugh Map

- Design and verify the following circuits using Verilog HDL and Schematic
- Verilog
 - ◆ Behavioral level modeling
 - ◆ Dataflow modeling
 - ◆ Structural level modeling
- Schematic
- Please write and upload the lab report (Lab05) -- Due on 2022/10/07 23:59

Exercise 1

- Derive $(x \downarrow y) \downarrow z = (x + y)z'$, $z \downarrow (y \downarrow x) = z'(y + x)$ and $x \downarrow (y \downarrow z) = x'(y + z)$ (applying DeMorgan's theorem)
- Verify $(x \downarrow y) \downarrow z = z \downarrow (y \downarrow x)$ (using Structural level modeling)
- Verify $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$ (using Structural level modeling)

  

Exercise 2

- XOR is an odd function
- Complete the truth table of four-variable XOR function

$$F(w, x, y, z)$$

- $F1 = (w \oplus x) \oplus (y \oplus z)$

$$F2 = w \oplus (x \oplus (y \oplus z))$$

$$F3 = w \oplus x \oplus y \oplus z$$

- Verify $F1 = F2 = F3$
(using Structural level modeling)

w	x	y	z	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Exercise 3

- $F(w, x, y, z) = w'yz' + w'xy + wxz + xyz + wx'y'$
- Draw the Karnaugh map and find **all** the **simplest sum-of-products** of F
- If the simplest sum-of-products of F are $F4$, $F5$ and $F6$, verify $F4 = F5 = F6$ (using **Verilog Dataflow modeling**)

		yz			
		00	01	11	10
wx	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10