

DSLab. 04 Canonical and Standard Forms

Lab. 04 Canonical and Standard Forms

- Design and Verify the following circuits using Verilog HDL
- Schematic
- Verilog HDL
 - Behavioral level modeling
 - Dataflow modeling
 - Structural level modeling
- Please write and upload the lab report (Lab04) -- Due on 2022/09/30 23:59

Operators in Verilog

Table 8.1 *Verilog 2001 HDL Operators*

Operator Type	Symbol	Operation Performed	
Arithmetic	+	addition	
	-	subtraction	
	*	multiplication	
	1	division	
	%	modulus	
	**	exponentiation	
Bitwise or Reduction	~	negation (complement)	
	&	AND	
	I	OR	
	^	exclusive-OR (XOR)	
Logical	1	negation	
	&&	AND	
	II	OR	
Shift	>>	logical right shift	
	<<	logical left shift	
	>>>	arithmetic right shift	
	<<<	arithmetic left shift	
	{,}	concatenation	
Relational	>	greater than	
	<	less than	
	==	equality	
	!=	inequality	
	===	case equality	
	!==	case inequality	
	>=	greater than or equal	
	<=	less than or equal	

Table 8.2 *Verilog Operator Precedence*


+ -! ~ & ~& ~ ^ ~ ^ ^~ (unary)	Highest precedence	
**	I	
* / %		
+ - (binary)		
<< >> <<< >>>		
<<=>>=		
== != === !==		
& (binary)		
^ ^~ ~^ (binary)		
(binary)		
&&		
?: (conditional operator)	*	
{}{{}}	Lowest precedence	


Copyright ©2012 Pearson Education, publishing as Prentice Hall

Use parentheses to enforce your priority

Copyright ©2012 Pearson Education, publishing as Prentice Hall

 Example 1: Half Adder (Dataflow modeling)




 

$$S = A \oplus B$$
$$C = AB$$

```
module half_adder (S, C, A, B);
  output S, C;
  input A, B;
  assign S = A ^ B;
  assign C = A & B;
endmodule
```

 Example 2: Carry of Full Adder (Dataflow modeling)



$$C = xy + xz + yz$$


```
module C_FA (C, x, y ,z);
  output C;
  input x, y, z;

  assign C = x & y | x & z | y & z;
endmodule
```

Verilog Structural Model (Gate Level)

- Built-in gate primitives:
 - and, nand, nor, or, xor, xnor, buf, not, bufif0, bufif1, notif0, notif1
- Usage:
 - nand (out, in1, in2);
 2-input NAND without delay
 - and #2 (out, in1, in2, in3);3-input AND with 2 t.u. delay
 - not #1 N1(out, in);
 NOT with 1 t.u. delay and instance name
 - xor X1(out, in1, in2);
 2-input XOR with instance name
- Write them inside module, outside procedures

 Example 3: Half Adder (Structural level modeling)



Assuming:

• XOR: 2 t.u. delay


• AND: 1 t.u. delay

```
module half_adder (S, C, A, B);
output S, C;
input A, B;

xor #2 (S, A, B);
and #1 (C, A, B);
```

endmodule

 
Example 4: Carry of Full Adder (Structural level modeling)



```
module C_FA(C, x, y, z);
  output C;
  input x, y, z;
  wire n1, n2, n3;
  and (n1, x, y);
  and (n2, x, z);
  and (n3, y, z);
  or (C, n1, n2, n3);
```

endmodule

Testbench

 

```
module t_half_adder;
 reg A;
 reg B;
 wire S;
 wire C;
 half_adder UUT ( .A(A), .B(B), .S(S), .C(C) );
 initial begin
   A=1'b0; B=1'b0;
   #10 A=1'b0; B=1'b1;
   #10 A=1'b1; B=1'b0;
   #10 A=1'b1; B=1'b1;
   #10 $finish;
 end
endmodule
```

Exercise 1

- F1 = (x+z)(y'z'+yz)
- Find and show the complement of F1 (F2) using DeMorgan's theorem
- Verify F1' = F2 (using Dataflow modeling)

Exercise 2

- Find and show the sum of minterms (F3) of the following truth table
- Find and show the product of maxterms (*F4*) of the following truth table
- Verify F3 = F4 (using Structural level modeling)

W	X	У	Z	F
0	0	0	0	0
0 0 0 0 0 0 0	0	O	1	1
0	0	1	0	1
0	0	1	1	1
0		0	0	0
0	1 1	0		0 1
0	1	1	1 0	1
	1 1	1	1	0
1	0	0	1 0	0
1	0	0	1 0	0
1	0	1	0	0
1	0	1	$\frac{1}{0}$	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Exercise 3

- F5(x, y, z) = x+z'
- Find and show the canonical forms of F5, i.e., the sum of minterms (F6) and the product of maxterms (F7)
- Verify F5 = F6 = F7 (using Structural level modeling)