

Lab13

實驗主題: Design of Synchronous Sequential Logic

實驗日期:2022/11/28

學號姓名:B103040009 尹信淳

實驗內容: Design and Verify the following circuits using Verilog HDL

 


Table 5.11
State Table for Sequence Detector

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Exercise1:

Design a sequence detector to detect a sequence of three or more consecutive 1's in a string of bits coming through an input line (with D F/Fs)

Code:

Behavioral model

```

module ef_beh(
    output y,
    input x, clock, reset
);
    reg[1:0] state;
    parameter S0 = 2'b00, S1=2'b01, S2=2'b10, S3=2'b11;
    always @(posedge clock, negedge reset)
        if(reset==0) state<=S0;
        else case(state)
            S0:if(x) state<=S1; else state<=S0;
            S1:if(x) state<=S2; else state<=S0;
            S2:if(x) state<=S3; else state<=S0;
            S3:if(x) state<=S3; else state<=S0;
        endcase
    assign y = (state==S3);
endmodule
  
```

Structural model


```
module DFF(Q,Q_b,D,Clk,reset);
    output Q,Q_b;
    input D,Clk,reset;
    wire n1,n2,n3,n4;
    nand(n1,n4,n2);
    nand(n2,Clk,n1,reset);
    nand(n3,n2,Clk,n4);
    nand(n4,n3,D,reset);
    nand(Q,n2,Q_b);
    nand(Q_b,n3,Q,reset);
endmodule

module e1_struct(
    output y,
    input x,clock,reset
);
    wire A,B,A_b,B_b,n1,n2,n3,n4,DA,DB;
    and(n1,x,B);
    and(n2,x,A);
    and(n3,x,B_b);
    and(n4,x,A);
    or(DA,n1,n2);
    or(DB,n3,n4);
    DFF one(A,A_b,DA,clock,reset);
    DFF two(B,B_b,DB,clock,reset);
    and(y,A,B);
endmodule
```

Testbench:

```
module tb;
    wire y_beh, y_struct;
    reg x, clock, reset;
    e1_beh U0 (.y(y_beh), .x(x), .clock(clock), .reset(reset));
    e1_struct UUT (.y(y_struct), .x(x), .clock(clock), .reset(reset));
    initial #200 $finish;
    initial begin clock=0;forever#5 clock=~clock;end
    initial fork
    reset = 0;
    clock = 0;
    #5 reset=1;
    #10 x=0;
    #20 x=1;
    #30 x=1;
    #40 x=1;
    #50 x=1;
    #60 x=1;
    #70 x=0;
    #80 x=1;
    #90 x=1;
    #100 x=0;
    join
endmodule
```

波形圖:

 

Exercise1 實驗結果與分析:

功能正確，且兩種寫法輸出相同。

Exercise2:

Design a sequence detector to detect a sequence of three or more consecutive 1's in a string of bits coming through an input line(with T F/Fs)

Code:

Behavioral model

```
module e2_beh(  
    output y,  
    input x,clock,reset  
);  
    reg[1:0] state;  
    parameter S0 = 2'b00,S1=2'b01,S2=2'b10,S3=2'b11;  
    always @(posedge clock,negedge reset)  
        if(reset==0) state<=S0;  
        else case(state)  
            S0:if(x) state<=S1; else state<=S0;  
            S1:if(x) state<=S2; else state<=S0;  
            S2:if(x) state<=S3; else state<=S0;  
            S3:if(x) state<=S3; else state<=S0;  
        endcase  
    assign y = (state==S3);  
endmodule
```


Structural model

```
module DFF(Q,Q_b,D,Clk,reset);  
    output Q,Q_b;  
    input D,Clk,reset;  
    wire n1,n2,n3,n4;  
    nand(n1,n4,n2);  
    nand(n2,Clk,n1,reset);  
    nand(n3,n2,Clk,n4);  
    nand(n4,n3,D,reset);  
    nand(Q,n2,Q_b);  
    nand(Q_b,n3,Q,reset);  
endmodule  
module TFF(Q,Q_b,T,Clk,reset);  
    output Q,Q_b;  
    input T,Clk,reset;  
    wire n1;  
    xor(n1,T,Q);  
    DFF one(Q,Q_b,n1,Clk,reset);  
endmodule  
module e2_struct(  
    output y,  
    input x,clock,reset  
);  
    wire A,B,A_b,B_b,x_b,n1,n2,n3,n4,n5,TA,TB;  
    not(x_b,x);  
    and(n1,x_b,A);  
    and(n2,x,A_b,B);  
    and(n3,x_b,B);  
    and(n4,x,A_b);  
    and(n5,x,B_b);  
    or(TA,n1,n2);  
    or(TB,n3,n4,n5);  
    TFF one(A,A_b,TA,clock,reset);  
    TFF two(B,B_b,TB,clock,reset);  
    and(y,A,B);  
endmodule
```

Testbench:

```
module tb;
  wire y_beh, y_struct;
  reg x, clock, reset;
  e2_beh U0 (.y(y_beh), .x(x), .clock(clock), .reset(reset));
  e2_struct U1 (.y(y_struct), .x(x), .clock(clock), .reset(reset));
  initial #200 $finish;
  initial begin clock=0; forever #5 clock=~clock; end
  initial fork
    reset = 0;
    clock = 0;
    #5 reset=1;
    #10 x=0;
    #20 x=1;
    #30 x=1;
    #40 x=1;
    #50 x=1;
    #60 x=1;
    #70 x=0;
    #80 x=1;
    #90 x=1;
    #100 x=0;
  join
endmodule
```

波形圖:

 

Exercise2 實驗結果與分析:

功能正確，且兩種寫法輸出相同。

實驗心得

這次的實驗跟上周很類似，但這次 structural 的電路要自己依照 F/F 的特性畫出來，除此之外都跟上周一樣。