



DSLAb. 07 Karnaugh Map (2)


Lab. 07 Karnaugh Map (2)

- Design and Verify the following circuits using Verilog HDL and Schematic
- Verilog
 - ◆ Behavioral level modeling
 - ◆ Dataflow modeling
 - ◆ Structural level modeling
- Schematic
- Please write and upload the lab report (Lab07) -- Due on 2022/10/21 23:59

 Exercise 1

■ $F = (AB' + A'B)(C + D')$

- ◆ Implement F with AND-OR gates (denoted as $F1$)
- ◆ Implement F with multi-level NAND gate circuit (denoted as $F2$)
- ◆ Implement F with multi-level NOR gate circuit (denoted as $F3$)
- ◆ Verify $F1 = F2 = F3$ (using Verilog Structural level modeling)



(a) AND-OR gates

Exercise 2

- Simplify the following Boolean function using Karnaugh maps:
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$
- Find the simplest sum of products ($F4$) and draw its logic diagram (two-level implementation)
 - ◆ Implement $F4$ with two-level NAND gate circuit (denoted as $F5$)
 - ◆ $F6 = (F4)'$, implement $F6$ with two-level OR-NAND (OAI) circuit
 - ◆ Verify $F4 = F5 = F6$ (using Verilog Structural level modeling)

Exercise 3

- Simplify the following Boolean function using Karnaugh maps:
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$
- Find the simplest product of sums ($F7$) and draw its logic diagram (two-level implementation)
 - ◆ Implement $F7$ with two-level NOR gate circuit (denoted as $F8$)
 - ◆ Implement $F7$ with two-level AND-NOR (AOI) circuit (denoted as $F9$)
 - ◆ Verify $F7 = F8 = F9$ (using Verilog Structural level modeling)