

Lab12


實驗主題: Analysis of Synchronous Sequential Logic

實驗日期: B103040009 尹信淳


實驗內容: Analyze and Verify the circuits using Verilog HDL

 Exercise1:

Simulate the sequential circuit shown in Fig. 5.17




Input equation & state equation:

 

State table & state diagram:

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

Code:

Behavioral modeling:

```

module exercise1(output out,input x,y,Clock,reset);
    reg A;
    parameter S0=1'b0, S1=1'b1;
    always @ (posedge Clock,negedge reset)
        if(reset==0)    A <= S0;
        else case(A)
            S0:if(x==0&&y==0 || x==1&&y==1) A<=A;else A<=S1;
            S1:if(x==0&&y==0 || x==1&&y==1) A<=A;else A<=S0;
        endcase
    assign out = A;
endmodule

```


Testbench:

```

module tb;
    wire out;
    reg x,y,Clock,reset;
    exercisel UUT (.out(out),.x(x),.y(y),.Clock(Clock),.reset(reset));
    initial #100 $finish;
    initial begin Clock = 0; forever #5 Clock = ~Clock; end
    initial fork
        reset=0;
        #10 reset=1;
        #10 {x,y}=2'b00;
        #20 {x,y}=2'b01;
        #30 {x,y}=2'b11;
        #40 {x,y}=2'b10;
    join
endmodule

```

Result:

 

Structural modeling:

```

module DFF(Q,Q_b,D,Clk,reset);
    output Q,Q_b;
    input D,Clk,reset;
    wire n1,n2,n3,n4;
    nand(n1,n4,n2);
    nand(n2,Clk,n1,reset);
    nand(n3,n2,Clk,n4);
    nand(n4,n3,D,reset);
    nand(Q,n2,Q_b);
    nand(Q_b,n3,Q,reset);
endmodule

module e1(A,A_b,x,y,Clock,reset);
    input x,y,Clock,reset;
    output A,A_b;
    wire n1;
    xor (n1,x,y,A);
    DFF d1(A,A_b,n1,Clock,reset);
endmodule

```


Testbench:

```

module tb;
    wire A,A_b;
    reg x,y, Clock, reset;
    e1 UUT (.A(A),.A_b(A_b), .x(x),.y(y), .Clock(Clock), .reset(reset));
    initial #100 $finish;
    initial begin Clock = 0; forever #5 Clock = ~Clock; end
    initial fork
        reset = 0;
        #20 reset = 1;
        #20 {x,y} = 2'b00;
        #30 {x,y} = 2'b01;
        #40 {x,y} = 2'b11;
        #50 {x,y} = 2'b10;
        #60 reset = 0;
        #70 {x,y} = 2'b00;
        #80 {x,y} = 2'b01;
        #90 {x,y} = 2'b11;
        #100 {x,y} = 2'b10;
    join
endmodule

```

Result:

 


Exercise1 實驗結果與分析:

功能正確，且兩種寫法輸出相同。

 Exercise2:

Simulate the sequential circuit shown in Fig. 5.18



Input equation & state equation:

exercise 2


input equation: $J_A = B$, $K_A = B \cdot x$
 $J_B = x$, $K_B = x \oplus A$ (JK F/F: $Q^+ = JQ' + K'Q$)

state equation: $A^+ = J_A A' + K_A' A = BA' + (x+B)A$ ✓
 $B^+ = J_B B' + K_B' B = xB' + (x \oplus A)B$

State table & state diagram:

Table 5.4
State Table for Sequential Circuit with JK Flip-Flops

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 

Code:

Behavioral modeling:

```

module e2(output[1:0] out,input in,clock,reset);
    reg[1:0] state;
    parameter S0 = 2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
    always @ (posedge clock,negedge reset)
        if(reset==0) state<=S0;
        else case(state)
            S0:if(!in) state<=S1; else state<=S0;
            S1:if(in) state<=S2; else state<=S3;
            S2:if(!in) state<=S3; else state<=S2;
            S3:if(!in) state<=S0; else state<=S3;
        endcase
    assign out = state;
endmodule

```


Testbench:

```

module tb;
    wire [1:0] out;
    reg in,clock, reset;
    e2 uut (.out(out),.in(in), .clock(clock), .reset(reset));
    initial #100 $finish;
    initial begin clock = 0; forever #5 clock = ~clock; end
    initial fork
        reset=0;
        #20 reset = 1;
        #20 in = 0;
        #40 in = 1;
        #50 in= 0;
        #60 in= 0;
    join
endmodule

```

Result:

 

Structural modeling:

```


module DFF(Q,Q_b,D,Clk,reset);
    output Q,Q_b; input D,Clk,reset;
    wire n1,n2,n3,n4;
    nand(n1,n4,n2);
    nand(n2,Clk,n1,reset);
    nand(n3,n2,Clk,n4);
    nand(n4,n3,D,reset);
    nand(Q,n2,Q_b);
    nand(Q_b,n3,Q,reset); endmodule
module JKFF(Q,Q_b,J,K,Clk,reset);
    output Q,Q_b; input J,K,Clk,reset;
    wire n1,n2,n3,n4;
    and(n1,J,Q_b);
    not(n2,K);
    and(n3,n2,Q);
    or(n4,n1,n3);
    DFF d1(Q,Q_b,n4,Clk,reset); endmodule
module e2(A,B,x,clock,reset);
    output A,B; input x,clock,reset;
    wire x_not,B_not,n1,n2,n3,n4;
    not(x_not,x);
    and(n1,B,x_not);
    xor(n2,A,x);
    JKFF jk1(A,n3,B,n1,clock,reset);
    JKFF jk2(B,n4,x_not,n2,clock,reset);
endmodule

```

Testbench:

```
module tb;
    wire A,B;
    reg x,clock, reset;
    e2 UUT (.A(A),.B(B),.x(x), .clock(clock), .reset(reset));
    initial #100 $finish;
    initial begin clock = 0; forever #5 clock = ~clock; end
    initial fork
        reset=0;
        #20 reset = 1;
        #20 x = 0;
        #40 x = 1;
        #50 x = 0;
        #60 x = 0;
    join
endmodule
```

Result:

 

Exercise2 實驗結果與分析:

功能正常，且兩種寫法輸出相同

實驗心得

這次實驗開始練習較為複雜的序向電路，兩個 exercise 做的事情是一樣的。拿到電路圖之後，我們要先進行分析：先得出該電路中 F/F(s)的 input equation 及 next-state equation，隨後再依照該電路使用的 F/F 種類來得出 state diagram 或 state table。如此一來就能依照 state diagram(table)來進行 Behavioral modeling。除此之外，每題還需要用 Structural modeling 來驗證兩種 modeling 會得到相同結果。這兩題訓練了序向電路分析步驟，以及如何使用分析出來的 state diagram 來進行 behavioral modeling 的模擬。是個寶貴的實作經驗。