



# ***DSLAb.14 Registers & Counters***

# Lab. 14 Registers & Counters

- Design and Verify the following circuits using Verilog HDL
  - ◆ Four-bit universal shift register
  - ◆ BCD synchronous counter
- Please write and upload the lab report (Lab14) -- Due on 2022/12/09 23:59

# Example 1: State Diagram-Based HDL Model (Moore) (1/4)


 


Fig. 20

Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

# Example 1: State Diagram-Based HDL Model (Moore) (2/4)

## Structural model (Fig. 20)

```
module Moore_Model_STR_Fig_5_20 (  
    output y_out, A, B,  
    input x_in, clock, reset  
);  
    wire A, TB;  
  
    // Flip-flop input equations  
    assign TA = x_in & B;  
    assign TB = x_in;  
    //output equation  
    assign y_out = A & B;  
    // Instantiate Toggle flip-flops  
    Toggle_flip_flop_3 M_A (A, TA, clock, reset);  
    Toggle_flip_flop_3 M_B (B, TB, clock, reset);  
  
endmodule
```

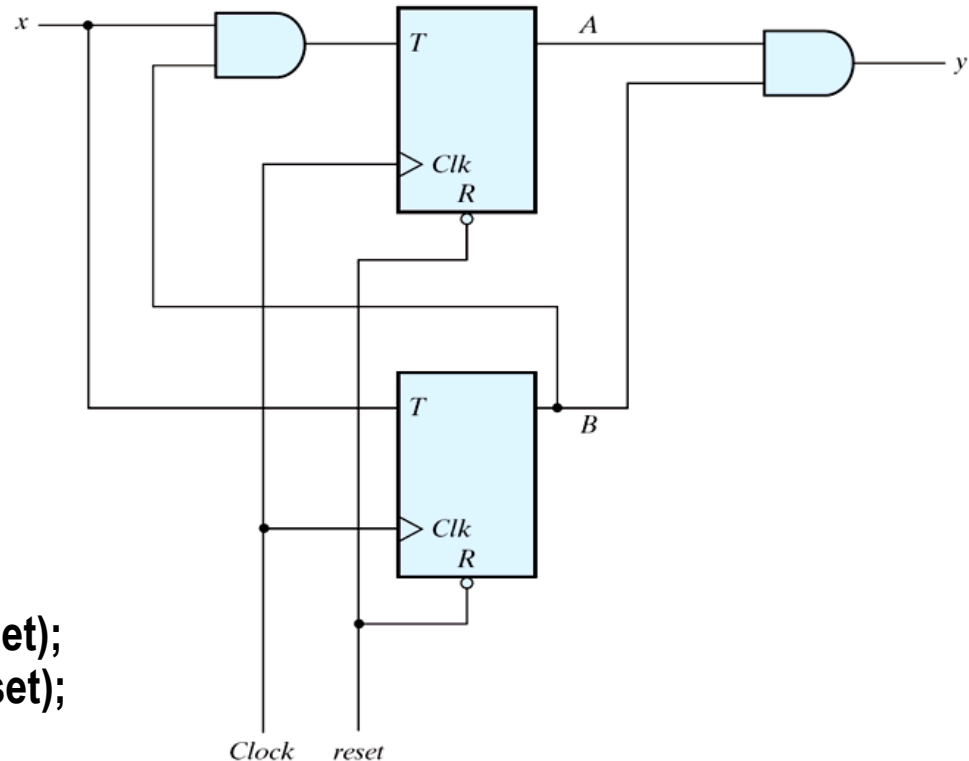


Fig. 20

# Example 1: State Diagram-Based HDL Model (Moore) (3/4)

## Behavioral model (State diagram)

```
module Moore_Model_Fig_5_20 (  
    output  y_out,  
    input   x_in, clock, reset  
);  
    reg [1: 0] state;  
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;  
  
    always @ (posedge clock, negedge reset)  
        if (reset == 0) state <= S0; // Initialize to state S0  
        else case (state)  
            S0: if (x_in) state <= S1; else state <= S0;  
            S1: if (x_in) state <= S2; else state <= S1;  
            S2: if (x_in) state <= S3; else state <= S2;  
            S3: if (x_in) state <= S0; else state <= S3;  
        endcase  
  
    assign y_out = (state == S3); // Output of flip-flops  
endmodule
```

 


Fig. 5.20

Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

# Example 1: State Diagram-Based HDL Model (Moore) (4/4)

```
module t_Moore_Fig_5_20;  
  wire    t_y_out_2, t_y_out_1;  
  reg     t_x_in, t_clock, t_reset;
```

```
  Moore_Model_Fig_5_20 M1 (t_y_out_1, t_x_in, t_clock, t_reset);  
  Moore_Model_STR_Fig_5_20 M2 (t_y_out_2, A, B, t_x_in, t_clock, t_reset);
```

```
  initial #200 $finish;  
  initial begin  
    t_reset = 0;  
    t_clock = 0;  
    #5 t_reset = 1;  
    repeat (16)  
      #5 t_clock = ~t_clock;
```

```
  end  
  initial begin  
    t_x_in = 0;  
    #15 t_x_in = 1;  
    repeat (8)  
      #10 t_x_in = ~t_x_in;
```

```
  end
```

```
endmodule
```

## Example 2: 4-bit universal shift register (1/3)

 


Fig. 6.7  
Four-bit universal shift register

**Table 6.3**  
*Function Table for the Register of Fig. 6.7*

Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


## Example 2: 4-bit universal shift register (2/3)

### Behavioral model

// **Behavioral description** of a 4-bit universal shift register  
// Fig. 6.7 and Table 6.3

```
module Shift_Register_4_beh (  
    output reg [3: 0] A_par,           // Register output  
    input [3: 0] I_par,               // Parallel input  
    input s1, s0,                     // Select inputs  
    MSB_in, LSB_in,                  // Serial inputs  
    CLK, Clear_b                      // Clock and Clear_b  
);
```

```
always @ (posedge CLK, negedge Clear_b)  
    if (~Clear_b) A_par <= 4'b0000;  
    else  
        case ({s1, s0})  
            2'b00: A_par <= A_par;           // No change  
            2'b01: A_par <= {MSB_in, A_par[3: 1]}; // Shift right  
            2'b10: A_par <= {A_par[2: 0], LSB_in}; // Shift left  
            2'b11: A_par <= I_par;           // Parallel load of input  
        endcase  
    endmodule
```

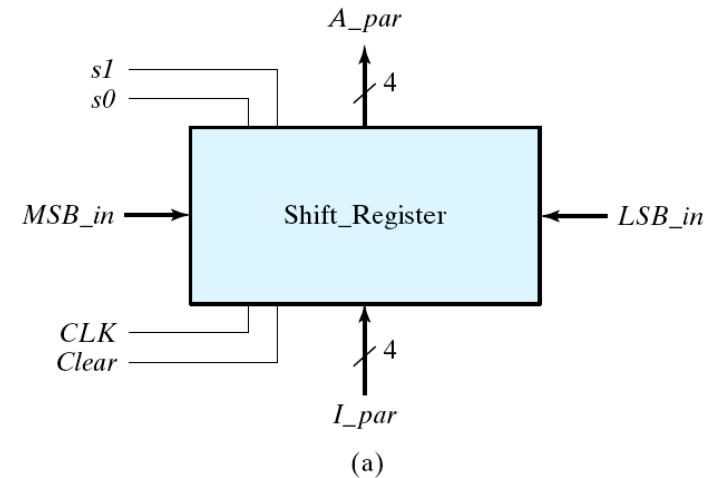

**Table 6.3**  
*Function Table for the Register of Fig. 6.7*

Mode Control		Register Operation
s <sub>1</sub>	s <sub>0</sub>	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load



## Example 2: 4-bit universal shift register (3/3)

```
module t_Shift_Register_4_beh ();
    reg          s1, s0,          // Select inputs
                MSB_in, LSB_in,  // Serial inputs
                clk, reset_b;     // Clock and Clear_b

    reg [3: 0]    I_par;          // Parallel input
    wire [3: 0]   A_par;          // Register output

    Shift_Register_4_beh M0 (A_par, I_par, s1, s0, MSB_in, LSB_in, clk, reset_b);

    initial #200 $finish;
    initial begin clk = 0; forever #5 clk = ~clk; end

    initial fork
        // test reset action load
        #3 reset_b = 1;
        #4 reset_b = 0;
        #9 reset_b = 1;

        // test parallel load
        #10 I_par = 4'hA;
        #10 {s1, s0} = 2'b11;

        // test shift right
        #30 MSB_in = 1'b0;
        #30 {s1, s0} = 2'b01;

        // test shift left
        #80 LSB_in = 1'b1;
        #80 {s1, s0} = 2'b10;

        // test circulation of data
        #130 {s1, s0} = 2'b11;
        #140 {s1, s0} = 2'b00;

        // test reset on the fly
        #150 reset_b = 1'b0;
        #160 reset_b = 1'b1;
        #160 {s1, s0} = 2'b11;


    join
endmodule
```

# Example 3: 4-bit ripple counter (1/2)


**Table 6.4**  
*Binary Count Sequence*

$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

**Fig. 6.8**  
Four-bit binary ripple counter

 

(a) With  $T$  flip-flops

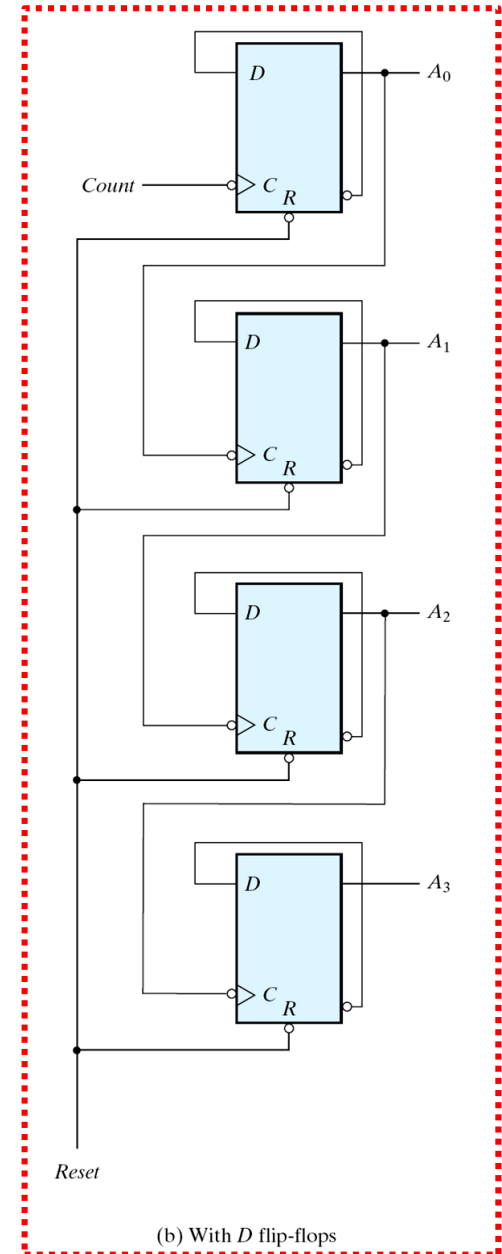

(b) With  $D$  flip-flops

## Example 3: 4-bit ripple counter (2/2)

### Structural model

```
`timescale 1ns / 100 ps
module Ripple_Counter_4bit (A3,A2,A1,A0, Count, Reset);
    output A3,A2,A1,A0;
    input Count,Reset;
//Instantiate complementing flip-flop
    Comp_D_flip_flop F0 (A0, Count, Reset);
    Comp_D_flip_flop F1 (A1, A0, Reset);
    Comp_D_flip_flop F2 (A2, A1, Reset);
    Comp_D_flip_flop F3 (A3, A2, Reset);
endmodule

//Complementing flip-flop with delay
//Input to D flip-flop = Q'
module Comp_D_flip_flop (Q, CLK, Reset);
    output Q;
    input CLK, Reset;
    reg Q;
    always @ (negedge CLK, posedge Reset)
        if (Reset) Q <= 1'b0; else Q <= #2 ~Q;
endmodule

//Stimulus for testing ripple counter
module testcounter;
    reg Count;
    reg Reset;
    wire A0,A1,A2,A3;
//Instantiate ripple counter
    Ripple_Counter_4bit M0 (A3, A2, A1, A0, Count, Reset);
    always
        #5 Count = ~Count;
    initial
        begin
            Count = 1'b0;
            Reset = 1'b1;
            #4 Reset = 1'b0;
        end
    initial #170 $finish;
endmodule
```

# Exercise 1: Four-bit universal shift register

- Design and verify the four-bit universal shift register using Verilog HDL
  - ◆ structural (gate-level) modeling

 


Fig. 6.7 (a)  
Four-bit universal shift register

**Table 6.3**

*Function Table for the Register of Fig. 6.7*

Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

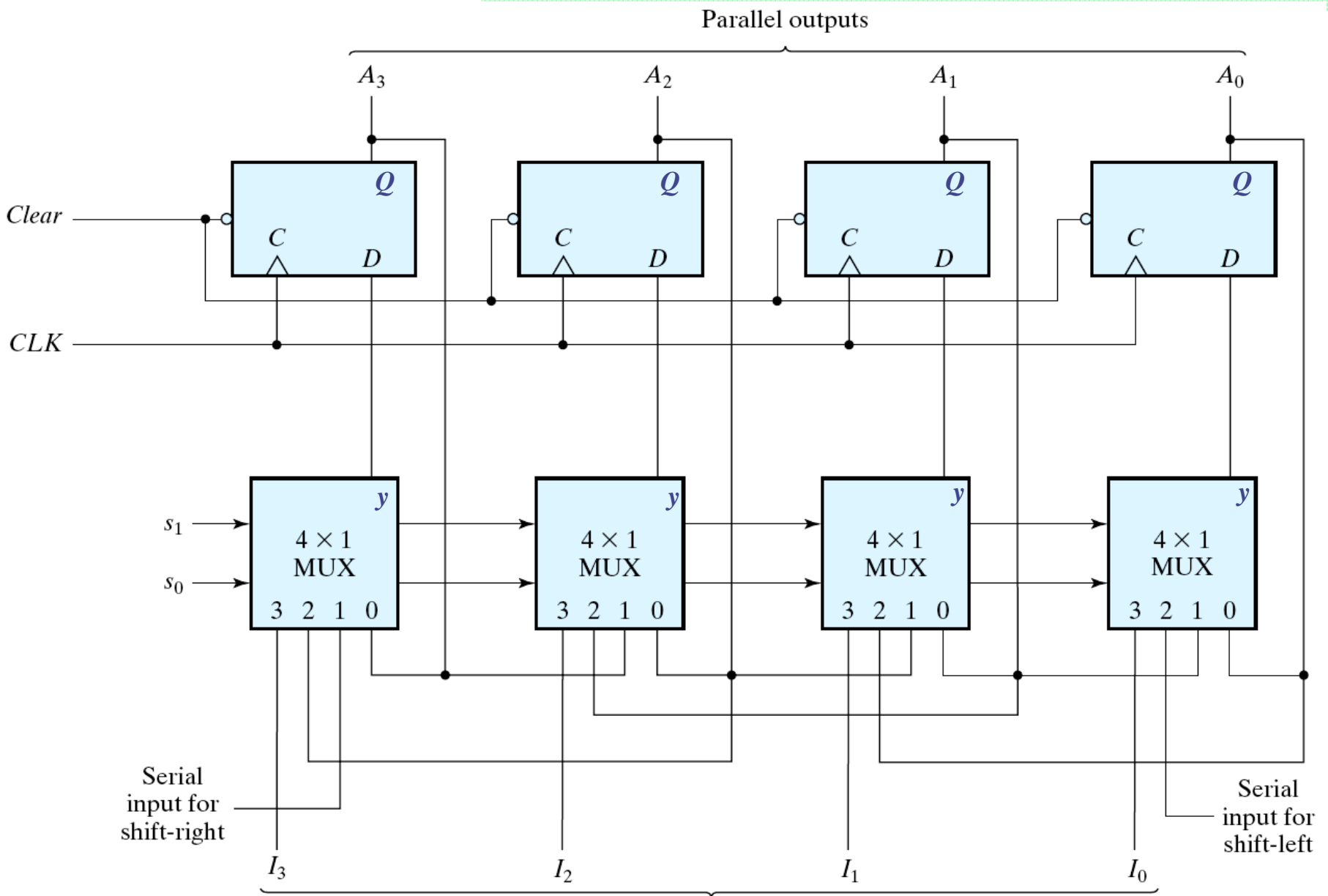


Fig. 6.7 Four-bit universal shift register  
(continued)

(b)

## Exercise 2: BCD synchronous counter (1/2)

- Design and verify the BCD synchronous counter using T flip-flops with asynchronous reset and Verilog HDL
  - ◆ structural (gate-level) modeling

 


Fig. 6.9 State diagram of a decimal BCD counter

## Exercise 2: BCD synchronous counter (2/2)

■ Simplified functions:

$$T_{Q1} = 1$$

$$T_{Q2} = Q_8'Q_1$$

$$T_{Q4} = Q_2Q_1$$

$$T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$

$$y = Q_8Q_1$$

**Table 6.5**  
*State Table for BCD Counter*

Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$TQ_8$	$TQ_4$	$TQ_2$	$TQ_1$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1